
# FFS ARDUINO CONNECTIONS
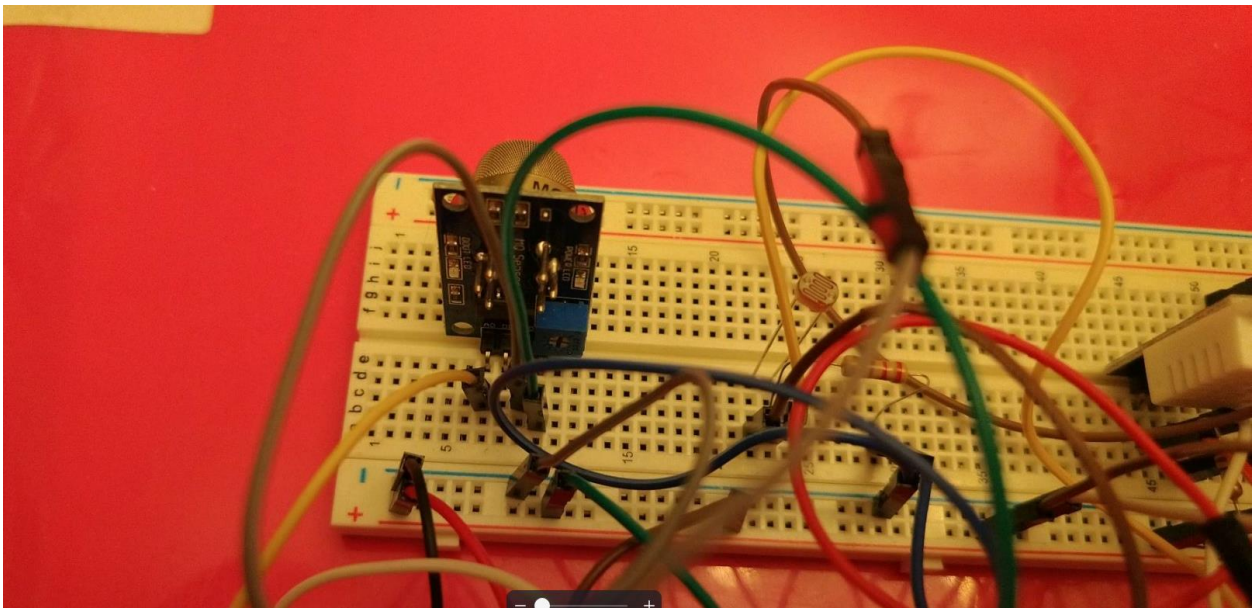
## FOLLOW: FINAL_CODE_3


1- mq135 gas sensor

A0 - analogue pin A0
DO - empty
GND - ground
VCC- vcc



2- LDR

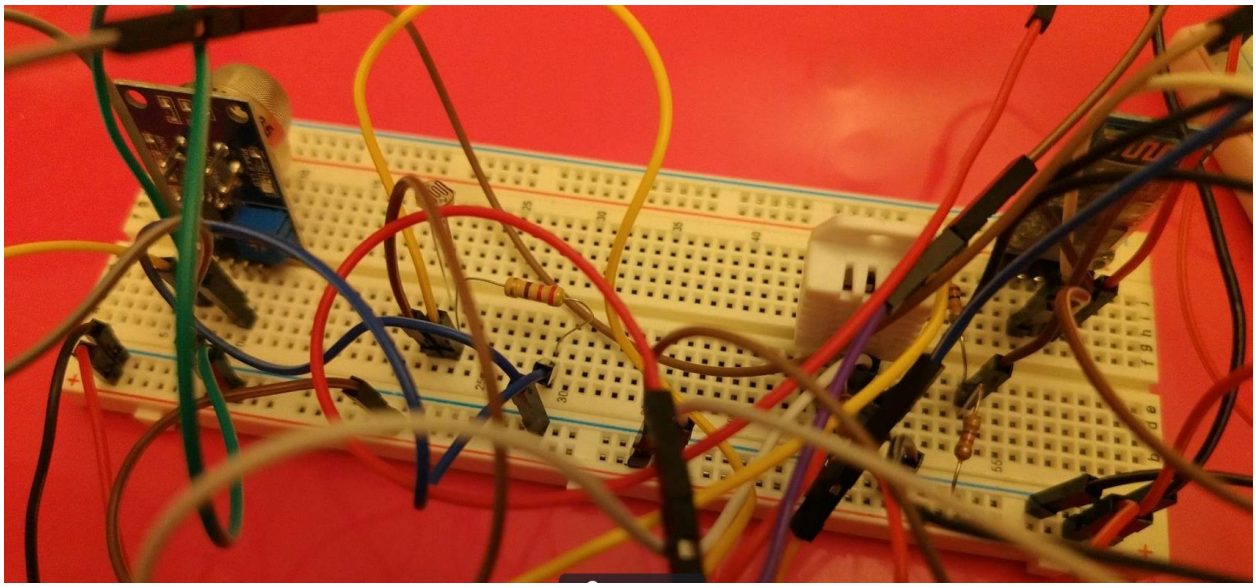1st pin - VCC
2nd pin - 220 ohms to GND
- A2 analogue pin




3- DHT 22

+ => VCC

Out => Digital pin 3


& 1 K ohms to VCC

- => GND

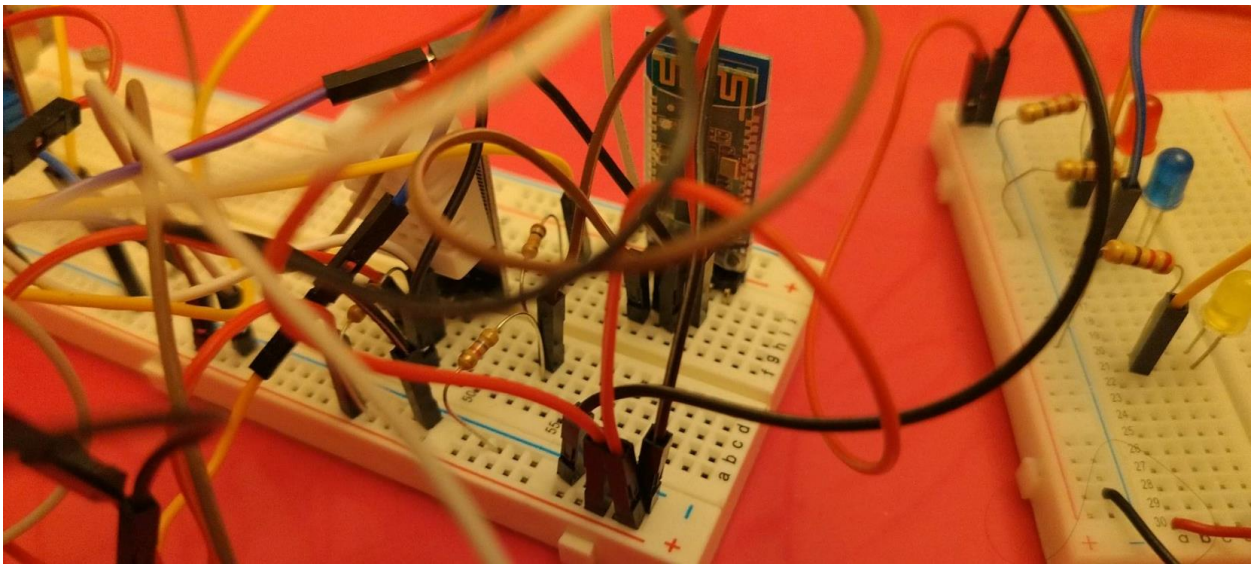


4 - LCD

GND - GND
VCC - VCC
SDA - A4
SCL - A5

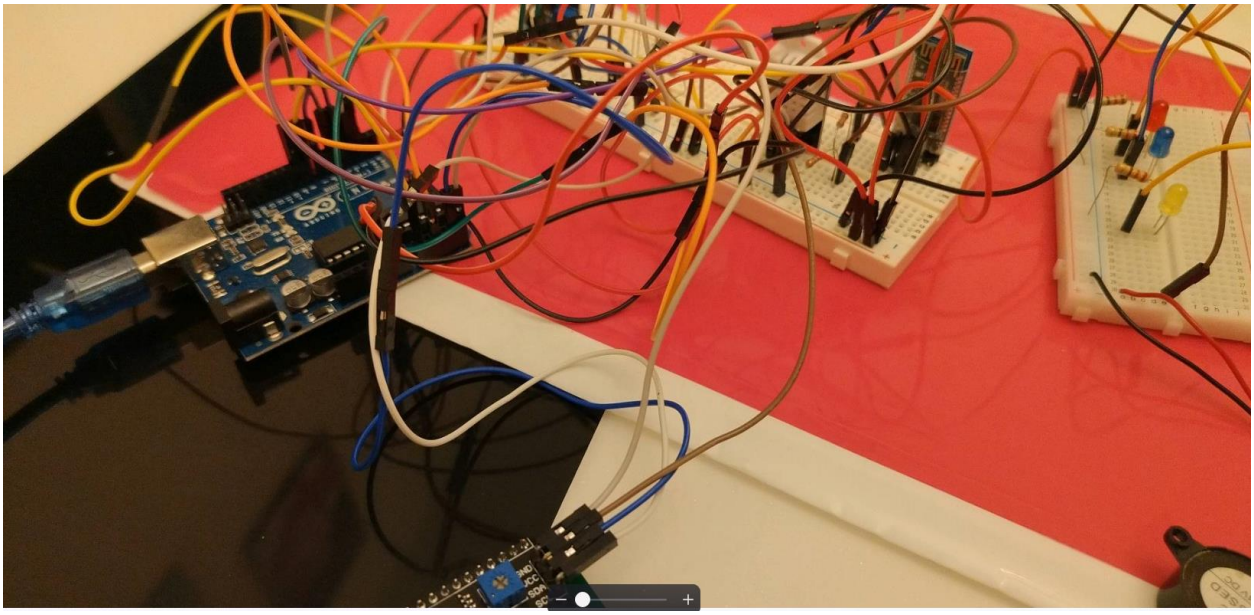

5- LED

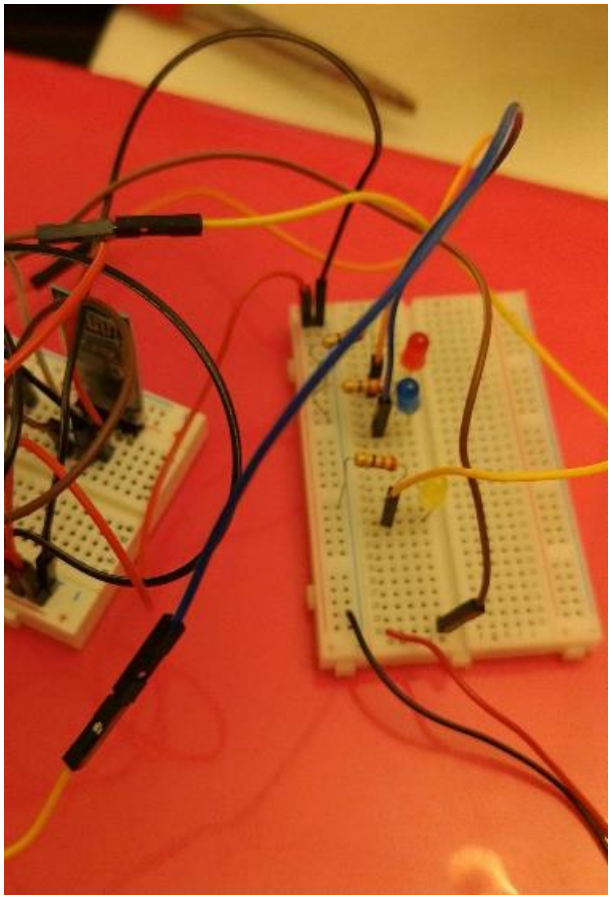

+ red :
-short- 220 to GND
- long - 4

+ blue :
- short - 220 to GND
- long - 2

+ yellow :
- short - 220 to GND
- long – 5

6- buzzer
Black - GND

Red - 7

